

### Question A

1.  $3.4 \mu\text{A}$

$0.61 \text{ cm}^2$

$4.5 \cdot 10^{15} \text{ Photons/s} \cdot \text{cm}^2 \rightarrow 4.5 \cdot 10^{13}$

$3.4 \cdot 10^{-6} \text{ A} \rightarrow \text{Coulomb/s}$

$$\frac{3.4 \cdot 10^{-6}}{1.6 \cdot 10^{-19}} = 2.125 \cdot 10^{13} \text{ Photons/s}$$

$$2.125 \cdot 10^{13} = x \cdot 4.5 \cdot 10^{13}$$

$$x = 0.47$$

$$x = 47\%$$

$I \cdot Q = \text{flux}_e$   
 $P_{\text{win}} = \text{flux} \cdot E$

2. ?

### Question B:

1.  $0.050 \text{ A}$

$21 \text{ V}$

$43\%$

$$P_{\text{tot}} = P_{\text{heat}} + P_{\text{win}}$$

$$P_{\text{heat}} = P_{\text{tot}} \cdot Q$$

$$P_{\text{heat}} = 0.05 \cdot 21 \cdot 0.43$$

$$P_{\text{heat}} = 0.04515$$

$$P_{\text{win}} = 45 \text{ mW}$$

2.  $P_{\text{win}} = \text{flux} \cdot E$

$$I \cdot Q = \text{flux}_e$$

$$\text{flux} = \frac{P_{\text{win}}}{E}$$

$$\text{flux} = \frac{0.045}{1.985 \cdot 10^{-16} \cdot 550}$$

$$\left( \frac{0.045}{1.985 \cdot 10^{-16} \cdot 550} \right) = Q$$

$$Q = 0.3994 = 40\%$$

### Question C:

1.  $6.6 \cdot 10^{-11}$

$$n_p = n_i^3$$

$$n_i = 1.5 \cdot 10^{10} / \text{cm}^3$$

$$P_e = \frac{1}{q \cdot (P_{\text{up}} + n_i e)}$$

On peut dire que  $P \approx 0$

Une échelle pour nmes

$$P_e = \frac{1}{q \cdot (n \cdot 950)}$$

$$6.6 \cdot 10^{-11} = \frac{1}{1.6 \cdot 10^{-19} \cdot (n \cdot 950)}$$

$$n = 9.95 \cdot 10^{16}$$

$$10 \cdot 10^{18} \text{ ou } 10^{19}$$

2. Oui, on peut négliger

3.  $0.00066$

### Question D

1.  $N_a = 10^{16}$

$N_d = 10^{17}$

$C_{\text{ss}} = 52.6 \cdot 10^{-9}$

$V_A = 9$

$m = 1/2$

$$C_s = C_{\text{ss}} \cdot \left( 1 + \frac{V_A}{V_0} \right)^m$$

$$C_s = \frac{52.6 \cdot 10^{-9}}{\left( 1 + \frac{9}{0.754277} \right)^{1/2}}$$

$$C_s = 1.46 \cdot 10^{-9}$$

$$V_0 = V_1 \ln \left( \frac{N_p N_d}{n_i^2} \right)$$

$$V_0 = 0.0259 \cdot \ln \left( \frac{10^{16} \cdot 10^{17}}{(1.5 \cdot 10^{10})^2} \right)$$

$$V_0 = 0.754277$$

### Question 1:

a)	$B = 30$	$I_B$	$V_B$	$I_B = 33.7 \mu A$	$V_B = 0$
	$V_T = 26 mV$	$I_C$	$V_C$	$I_C = 1 mA$	
	$ V_{BE}  > 0.7 V$	$I_E$	$V_E$	$I_E = 1 mA$	

$$0 - V_{BE} - V_{RE} - V_{MA} = 0$$

$$0 - V_{BE} - R_2 I_B (B+1) - V_{MA} = 0$$

$$0 - 0.7 - 2200 \cdot I_B (30+1) - 3 = 0$$

$$I_B = 0.00003372 = 33.7 \mu A$$

$$I_E = I_B (B+1) = 0.00104 = 1 mA$$

$$I_C = I_E - I_B = 0.00104 - 0.00003372 = 0.00100628$$

$$-3 + R_2 I_E = V_E$$

$$-3 + 2200 \cdot 0.00104 = -0.712 V = V_E$$

$$3 - R_1 I_C = V_C$$

$$3 - 2200 \cdot 0.00104 = 0.786184 = V_C$$

**b)**

$V_{TP} - V_{A3} - V_{BE} = 0$	$I_B = 74 \mu A$	$V_B = 0$
$3 - R_2 I_B (B+1) - 0.7 = 0$	$I_C = 222 nA$	$V_E = 0.7$
$I_B = 74 \mu A$	$I_E = 23 nA$	$V_C = -0.774$
$I_E \cdot I_B (B+1) = 0.0023 \cdot 23 \mu A$		
$I_C \cdot I_E - I_B = 0.002226 - 222 nA$		

$$V_E = -0.7 \quad V_{BE} = V_B - V_E$$

$$V_B = 0$$

$$V_C = -3 + 1 \cdot 0.002226 = -0.774$$

**c)**

$I_D = 0.00115 A$	$V = RI$	$R = 3043.478 \Omega$
$V_T = -0.7 V$	$\frac{3.5}{0.00115} = 3043.478$	
$n_p C_{ox} = 60 \text{ } nF/V^2$		
$L = 0.8 \text{ } \mu m$	$I_D = \frac{1}{2} K (V_{DS} - V_t)^2$	
$\lambda = 0$	$K = 0.00115 = \frac{1}{2} K ((3.5 - 0.7) - 0.7)^2$	
$V_{DS} = 3.5$	$K = 0.00359375$	
	$0.00359375 = 60 \cdot \left(\frac{w}{L}\right)$	
	$w = 47.916 \text{ } \mu m$	


### Question 2:

$$I_D = 2 A$$

$$V_{GS} = 4 V$$

$$V_{BS} = 0.9 V$$

### Question 3:

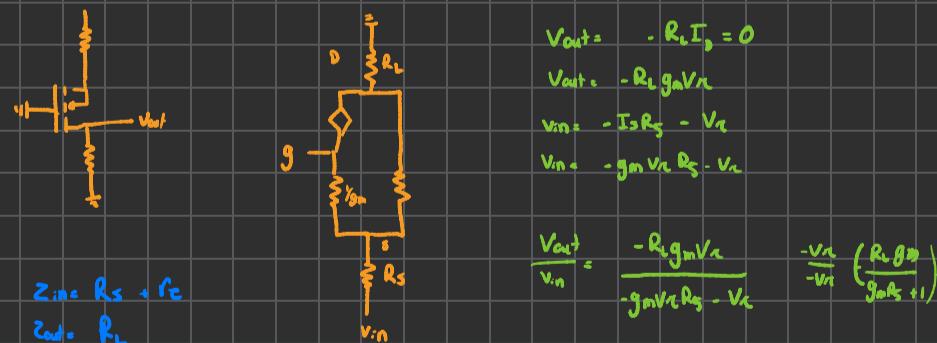

$$V_{out} = -R_L I_D = 0$$

$$V_{out} = -R_L g_m V_R$$

$$V_R = -I_D R_S = V_R$$

$$V_{in} = -g_m V_R R_S - V_R$$

$$\frac{V_{out}}{V_{in}} = \frac{-R_L g_m V_R}{-g_m V_R R_S - V_R} = \frac{-V_R}{R_S + R_L} \left( \frac{R_L}{g_m R_S + 1} \right)$$

### Question 4:

$V_{GS}$	$V_B$	$I_B$	$V_{GS} = 2.1968 V$
$V_{PS}$	$V_C$	$I_C$	$V_{PS} = 7.6468 V$
$I_B = I_S$	$V_E$	$I_E$	$I_D = 2.2920 mA$

on a planer,  $q_0=1$  est  
on active,  $q_0=1$  est

$$V_g = 10 - \frac{1.8}{4} = 4.5$$

$$K = K \left( \frac{w}{l} \right)$$

$$K = 100 \cdot \frac{w}{l}$$

$$0.00383 = 3200 \cdot 10^{-6} (4.5 - 1)$$

$$0.00383 = \sqrt{2 \cdot 3200 \cdot 10^{-6} \cdot I_D}$$

$$I_D = 2.2920 mA$$

$$V_D = 10$$

$$V_{GS} = V_D - V_S$$

$$V_{PS} = 10 - (V_g - V_{GS})$$

$$V_{PS} = 10 - 4.5 + 2.1968$$

230532

$$V_s = V_B = 2.3032 \text{ V}$$

$$V_C = 10 - R_C I_C$$

$$V_E = 0 + R_E I_E$$

$$V_B = 2.3032$$

$$V_C = 8.4127 \text{ V}$$

$$V_E = 1.6029 \text{ V}$$

$$I_B = 4.07 \mu\text{A}$$

$$I_C = 4.07 \text{ mA}$$

$$I_E = 4.07 \text{ mA}$$

$$V_S - V_{BE} - R_E I_E = 0$$

$$2.3032 - 0.7 - 390 \cdot 0.00407 = 0$$

$$I_B = 4.07 \mu\text{A}$$

$$I_C = 4.07 \text{ mA}$$

$$I_E = 4.07 \text{ mA}$$

$$V_C = 10 - 390 \cdot 0.00407 = 8.4127$$

$$V_E = 0 + 390 \cdot 0.00407 = 1.6029$$

b)  $R_1 \parallel R_2$

$$\frac{1}{\frac{1}{R_1} + \frac{1}{R_2}} = \frac{1}{\frac{1}{22k\Omega} + \frac{1}{990k\Omega}} = 990 \text{ k}\Omega$$

$$= 16 \text{ mHz}$$

$$= 7.26 \text{ Hz}$$

c)

Question 5:

a)



$$Z_{in} = R_C \parallel R_C$$

$$V_{in} = R_C \cdot I_C$$

$$Z_{out} = R_C \parallel R_L$$

$$V_{out} = \alpha I_C (R_C \parallel R_L)$$

$$\frac{\alpha I_C (R_C \parallel R_L)}{R_C I_E} = \frac{\alpha (R_C \parallel R_L)}{R_C} = \frac{\alpha}{R_C} = g_m$$

$$g_m (R_C \parallel R_L)$$

c)  $r_o \uparrow \quad r_h \uparrow \quad s_o \uparrow \quad g_m \uparrow$

